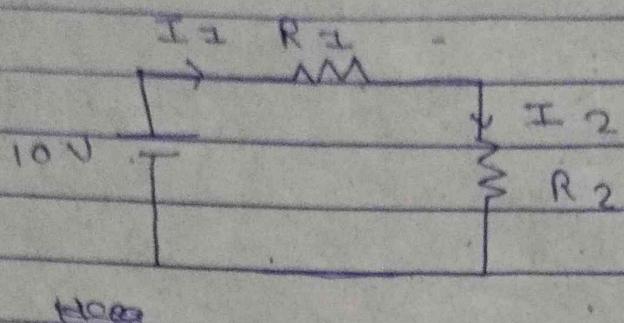


Problem:

i)



$$i) \quad R_1 = 1\text{K}\Omega \quad R_2 = 2\text{K}\Omega$$

Applying KVL $10 - 1\text{K}I_1 - 2\text{K}I_2 = 0$

Here $I_1 = I_2$ because $I_1 = I_2 = I$

~~$$10 - 1\text{K}I - 1\text{K}I = 0$$~~

$$10 - 2\text{K}I = 0$$

$$10 = 2\text{K}I$$

$$I = \frac{10}{2\text{K}} = 5\text{mA}$$

ii) $R_1 = 1\text{K}\Omega \quad R_2 = 10\text{K}\Omega$

Applying KVL $I_1 = I_2 = I$

$$10 - 1\text{K}I - 10\text{K}I = 0$$

$$10 - 11\text{K}I = 0$$

$$11\text{K}I = 10$$

$$I = \frac{10}{11\text{K}} = 0.9\text{mA}$$

$$(ii) R_1 = 1\text{ k}\Omega \quad R_2 = 5\text{ k}\Omega$$

Applying KVL $10 - 1\text{ k}\Omega I - 5\text{ k}\Omega I = 0$

$$10 = 6\text{ k}\Omega I$$

$$I = \frac{10}{6\text{ k}\Omega}$$


$$= 1.67 \text{ mA}$$

$$(iv) R_1 = 1\text{ k}\Omega \quad R_2 = 100\text{ k}\Omega$$

Applying KVL $10 = 1\text{ k}\Omega I - 100\text{ k}\Omega I = 0$

$$10 = 101\text{ k}\Omega I$$
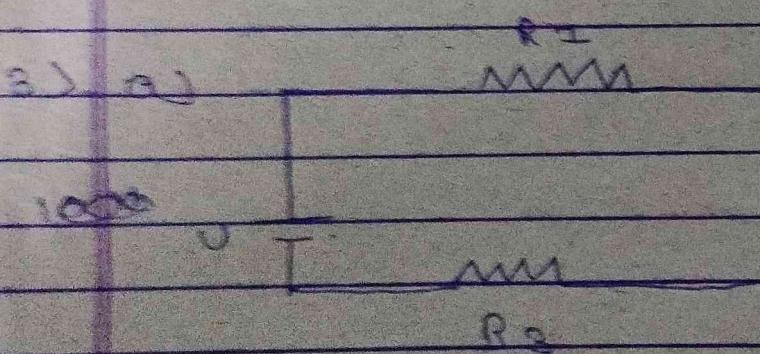
$$I = \frac{10}{101\text{ k}\Omega} = 0.099 \text{ mA}$$



$$\text{Given } V = 10 \text{ V}, R_1 = 1\text{ k}\Omega, R_2 = 100\text{ k}\Omega, R_3 = 1\text{ k}\Omega$$

$$10 - I R_1 - I R_2 - I R_3 = 0 \quad V_{R_1} = 3.33 \text{ V}$$

$$10 - 1\text{ k}\Omega I - 100\text{ k}\Omega I - 1\text{ k}\Omega I = 0 \quad V_{R_2} = 3.33 \text{ V}$$

$$10 - 3\text{ k}\Omega I = 0 \quad V_{R_3} = 3.33 \text{ V}$$

$$I = \frac{10}{3\text{ k}\Omega} = 3.33 \text{ mA}$$

b) $V = 10V$, $R_1 = 1K$, $R_2 = 2K$, $R_3 = 4K$

$$10 - 1KI - 2KI - 4KI = 0$$

$$10 - 7KI = 0$$

$$10 = 7KI$$

$$I = \frac{10}{7} = 1.428 \text{ mA}$$

$$VR_1 = IR_1 = 1.428 \times 1K = 1.428 \text{ V}$$

$$VR_2 = IR_2 = 1.428 \times 2K = 2.856 \text{ V}$$

$$VR_3 = IR_3 = 1.428 \times 4K = 5.712 \text{ V}$$

c) $V = 10V$, $R_1 = 1K$, $R_2 = 10K$, $R_3 = 100K$

$$10 - 1KI - 10KI - 100KI = 0$$


$$10 = 111KI$$

$$I = \frac{10}{111K} = 0.09 \text{ mA}$$

$$VR_1 = 0.09 \text{ mA} \times 1K = 0.09 \text{ V}$$

$$VR_2 = 0.09 \text{ mA} \times 10K = 0.9 \text{ V}$$

$$VR_3 = 0 \text{ V}$$

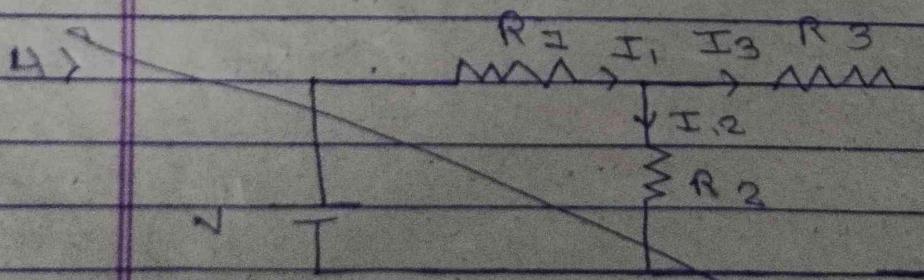

$$4 > ij \quad V = 5V, R_1 = 7K, R_2 = 10K, R_3 = 2K$$

$$\begin{aligned} R_{eq} &= R_1 + (R_2 || R_3) \\ &= 7K + (10K || 2K) \\ &= 2.67K \Omega \end{aligned}$$

$$\therefore I_2 = \frac{5}{2.67K} = 1.873 \text{ mA}$$

$$\begin{aligned} -I_3(2K) + 10K(I_2) &= 0 \\ 10KI_2 - 2KI_3 &= 0 \end{aligned}$$

$$\text{Now from KCL } I_1 = I_2 + I_3$$

$$\therefore I_2 + I_3 = 1.873 \text{ mA}$$

multiply by 2 : $2I_2 + 2I_3 = 3.746 \text{ mA}$

$$\text{Now } 10I_2 - 2I_3 = 0$$

$$2I_2 + 2I_3 = 3.746 \text{ mA}$$

$$12I_2 = 3.746$$

$$I_2 = 0.312 \text{ mA}$$

$$I_3 = 1.561 \text{ mA}$$

$$I_2 = 0.312 \text{ mA}$$

$$I_1 = 1.873 \text{ mA}$$

$$V_{R1} = 1.873V \quad V_3 = 3.122$$

$$V_{R2} = \cancel{3.122}$$

$$\cancel{0.312}$$

$$3.122V$$

b) $V = 5V \quad R_1 = 7\Omega \quad R_2 = 2\Omega \quad R_3 = 10\Omega$

$$R_{eq} = R_1 + (R_2 \parallel R_3)$$

$$= 7 + 1.67$$

$$= 8.67 \Omega$$

$$I_1 = \frac{5}{8.67\Omega} = 0.573 \text{ mA}$$

$$-I_3(10\Omega) + I_2(2\Omega) = 0$$

$$2I_2 - 10I_3 = 0$$

$$I_2 + I_3 = 0.573 \text{ mA}$$

$$10I_2 + 10I_3 = 5.73$$

$$10I_2 + 10I_3 = 18.73$$

$$2I_2 - 10I_3 = 0$$

$$12I_2 = 18.73$$

$$I_2 = 1.56 \text{ mA}$$

$$I_3 = 0.313 \text{ mA}$$

5> b) The reading are different in CRO and DMM because DMM shows rms value, where the CRO shows the waveform with peak value and $V_p = 52 \text{ V rms}$

c) The readings are different in CRO and DMM, because DMM shows rms value, where the CRO shows the waveform with peak value and $V_p = 55 \text{ V rms}$

6) $V = 2V$, $I_d = \text{TR}$, $R = 100\Omega$
 $V_d = ?$

Applying KVL $1 - 0.7 - I_d C100 = 0$

here $\text{TR} = I_d$ $0.3 = 100 I_d$
 $I_d = 3 \text{ mA} = \text{TR}$

$I_d = 3 \text{ mA}$ $V_d = 0.7 \text{ V}$
 $I_x = 3 \text{ mA}$

7) $V = 2V$, $I_d = \text{TR}$, $R = 10\Omega$
 $V_d = ?$

Applying KVL $1 - 0.7 - I_d C10 = 0$

here $\text{TR} = I_d$ $0.3 = I_d C10$
 $I_d = 30 \text{ mA}$

$I_d = 30 \text{ mA}$ $V_d = 0.7 \text{ V}$
 $I_x = 30 \text{ mA}$

8) $V = 5V$, $I_d = ?$, $I_x = ?$, $R = 10\Omega$
 $V_d = ?$

Applying KVL $5 - 0.7 - I_d C10 = 0$

here $I_d = 5x$ $4.3 = I_d C10$
 $I_d = 0.43 \text{ A}$

$$I_d = 0.43 \text{ A}, I_\pi = 0.43 \text{ A}, V_d = 0.7 \text{ V}$$

a) $V = 0.4 \text{ V}$ $I_d = 0$ $\bar{V}_D = 0$
 $V_d = 0.4 \text{ V}$

because $V_d = V_S$ till $V_S \leq 0.7$

$$I_d = I_\pi \text{ till } V_S \leq 0.7$$

(ii) a) $V = 7 \text{ V}$ $R = 100 \Omega$ $I_d = 0$

$$I_\pi = 0, I_d = 0, V_d = 10 \text{ V}$$

i. diode is in reverse bias.

b) $V = 10 \text{ V}$ $R = 100 \Omega$ $I_d = 0$

$$I_\pi = 0, V_d = 10 \text{ V}$$

c) $V = 50 \text{ V}$ $R = 100 \Omega$ $I_d = 0$


$$I_\pi = 0, V_d = 50 \text{ V}$$

d) $V = 100 \text{ V}$ $R = 100 \Omega$ $I_d = 0$

$$I_\pi = 0, V_d = 100 \text{ V}$$

if diode will replace with IN4007 then diode will burn out

7)

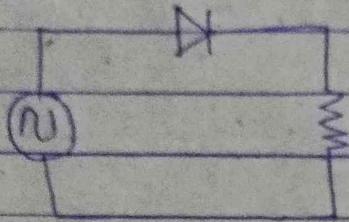

v_{in} - I_d I_x v_x - v_d

1) $10V_{P-P}$ 16.228 16.228 $2.21V$ 1.624
 \sin mA mA

2) $8V_P$ 23.137 23.137 2.756 2.314
 Triangle mA mA V

3) $200mV_P$ 2.371 2.371 231.123 166.664
 \sin mA mA uV mJ

9>a) Here $v_i = 230 \text{ rms} = 324.3 \text{ V}$
 $v_o = 5 \text{ V}$

$$\therefore n_i = n_i \Rightarrow n_i = \frac{324.3}{5} = 64.86$$

$$\frac{n_o}{n_o} = \frac{v_o}{v_i} = \frac{5}{324.3}$$

$$\therefore n_i = 65$$

$$n_o = 7$$

6) Here $v_i = 230 V_P - \text{rms} = 324.3 V$
 ~~$v_o = 5 V_C$ because it is center tap transformer therefore there is two section which gives output that is why we have to half our~~

$$2) V_i = 230 \text{ V rms} = 324.3 \text{ V peak}$$

$$V_o = 5 \text{ V peak}$$

$$\frac{N_i}{N_o} = \frac{V_i}{V_{o12}}$$

(because i_+ is center tap + transformer)

$$\frac{N_i}{N_o} = \frac{2V_i}{V_o}$$

~~$$324.3 = 2 \times 5$$~~

$$\frac{N_i}{N_o} = \frac{2 \times 324.3}{5}$$

$$N_i \approx 130$$

$$3) V_i = 314 \text{ V}, V_o = 9 \text{ V p}$$

$$\frac{N_i}{N_o} = \frac{V_i}{V_o}$$

$$\frac{N_i}{N_o} = \frac{314}{9} \Rightarrow N_i \approx 35$$

$$4) V_i = 100 \text{ V}, V_o = 6 \text{ V}$$

$$\frac{N_i}{N_o} = \frac{V_i}{V_o} \Rightarrow N_i = \frac{100}{6} = 33$$

center